


Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE FEBRUARY 1976/75c


A **PE TESTED!** FIRST!

Build the "TV DAZZLER"

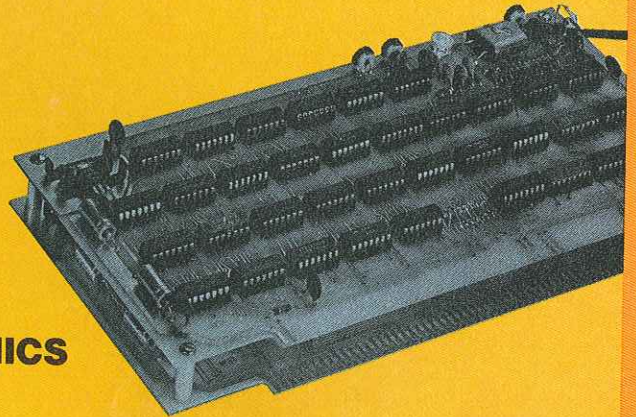COMPUTER ACCESSORY FOR PLAYING ACTION TV GAMES, DISPLAYING GRAPHICS AND ALPHANUMERICS ON COLOR TV




Light-Beam Communication Experiments

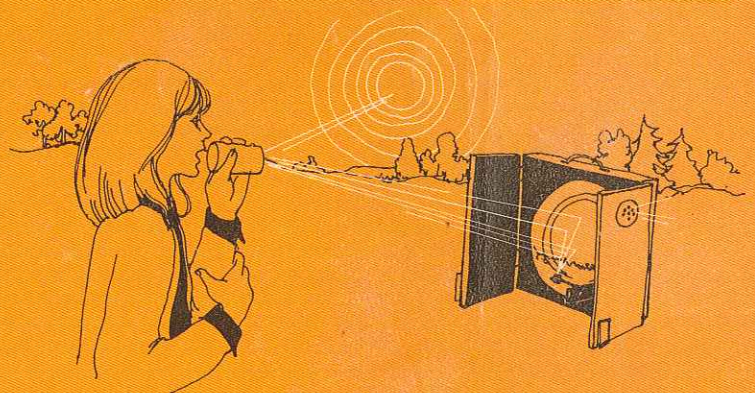

IT STARTED WITH ALEXANDER GRAHAM BELL

\$15 Temperature Meter

DO YOUR
TRANSISTORS
RUN TOO HOT?

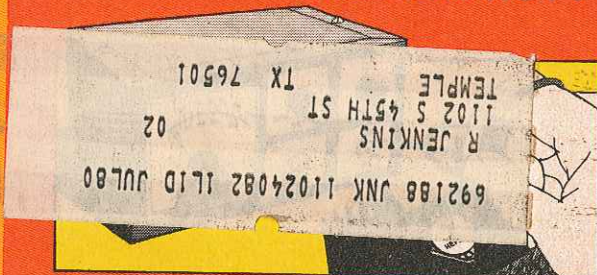

OTHER PROJECTS:

A High-Power Mobile Stereo Amp for Auto, Camper or Boat

Multi-Battery Charger Handles Four Cell Types Simultaneously

TEST REPORTS:

- Dual Stereo Cassette Deck
- Jensen Bookshelf Speaker System
- Browning "Golden Eagle" CB Base Station
- Triplett "Safety" VOM





The component look. By design.

Rather than adapt one transport design to fit another need, we produced a completely new, highly streamlined mechanism. From the inside out. It's called the A-400.

Twin rotary levers control the transport functions with smooth, positive cam action. Which means unnecessary mechanical linkages have been eliminated. You get peace of mind instead, because fewer moving parts assure greater reliability and long term dependability.

Since the cassette loads vertically into the A-400, the adverse effect of gravity on the cassette package itself is eliminated. So tape jams are prevented and smooth, even tape packs are predictable.

If new design concepts superbly executed appeal to you, put an A-400 through its paces. Just call (800) 447-4700* toll free for the name and location of your nearest TEAC retailer. You'll find that the A-400 delivers definitive TEAC performance with the added convenience of a front load component. All by design. *In Illinois, call (800) 322-4400.

A-400



TEAC® The leader. Always has been.

TEAC Corporation of America
7733 Telegraph Road, Montebello, Calif. 90640
©TEAC 1975

Popular Electronics®


FEBRUARY, 1976

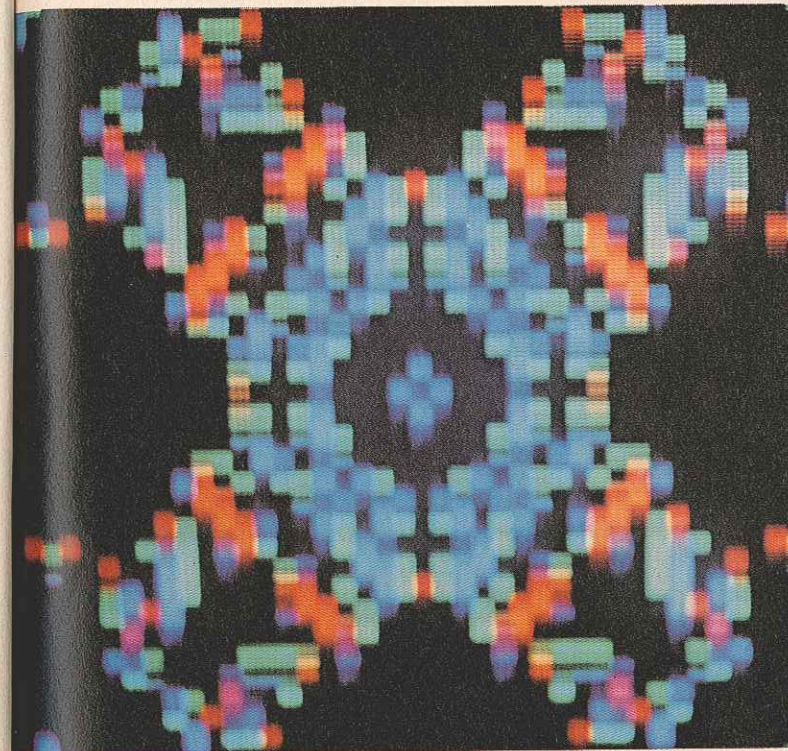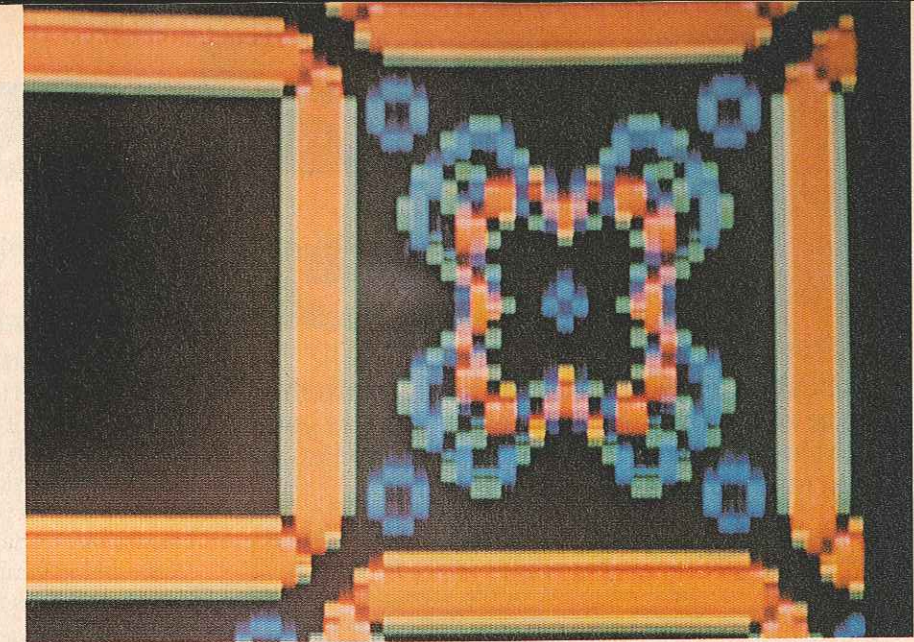BY TERRY WALKER,
ROGER MELEN,
HARRY GARLAND
ED HALL



BUILD THE TV DAZZLER

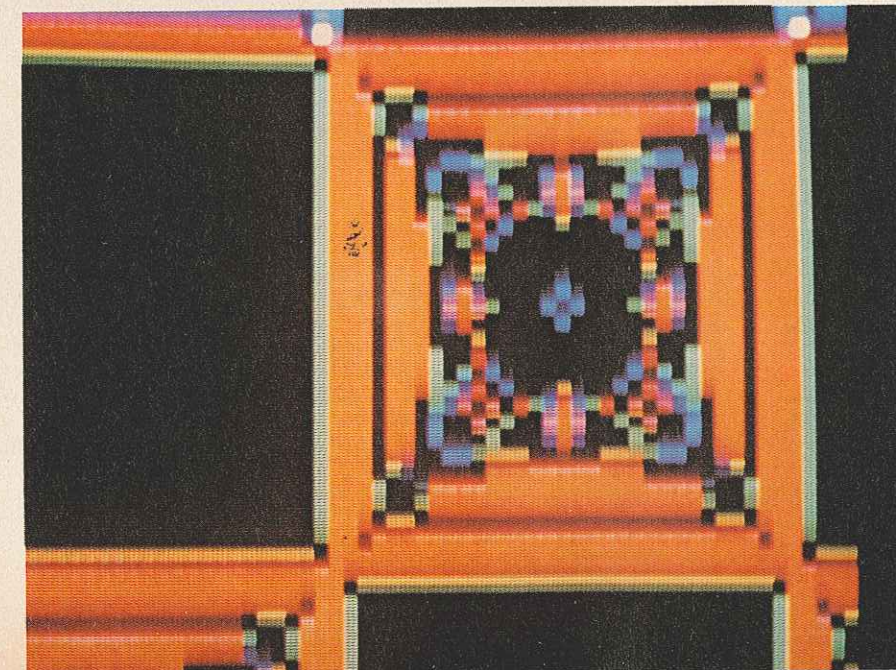*Unique computer accessory
provides alphanumerics
and graphics in full color.*



THE TV DAZZLER provides versatile electronic coupling between a small home computer and a color TV set. It can be used to generate action games, animated displays, educational learning drills, graphs, even light shows—all in *full color!* The Dazzler is designed to plug directly into the Altair 8800 computer (POPULAR ELECTRONICS, Jan. 1975); however, since it uses direct memory access (DMA) to scan the computer memory, it can easily be used with many other computers. If a Teletypewriter is your only communications link with your computer, here is a chance to build this new concept in computer peripherals at less than the

"Breaker . . . Breaker . . ."
**Break-through with
 BREAKER!**

The New Freedom Line of CB Mobile and Base Antennas and Accessories made in the U.S.A. for communications between people.

A wide selection of "revolutionary" new CB High Efficiency communications antennas of superior strength, electronically and physically, for all the talk power your CB rig will deliver—coming and going in the 27 Megahertz frequency band.

Mobile Breaker antennas for cars, trucks, trailers, sports cars, station wagons, motorcycles, boats. Breaker base station antennas to communicate with mobiles and hand helds . . . all designed specifically for the outstanding transmission and reception of CB signals.

The high quality and materials of the Breaker CB antennas and accessories assure you the maximum in performance for many years and at reasonable cost. Performance-tested Breaker CB antennas offer you these advantages plus more:

- ★ Easily adjust for lowest VSWR
- ★ Long-life stainless steel and fiberglass whips
- ★ Highest quality coaxial cable with solderless connections
- ★ Innovative engineering designs
- ★ Packaged for quick, easy installation to get you on the air fast, complete with cables and hardware

All Breaker antennas are American made in Arlington, Texas. In keeping with the tradition of the Bi-Centennial they are proudly named after our revolutionary heroes and places. Red, white and blue are also the colors of Breaker. Chosen because we too are very proud of our heritage and contribution to making exciting products for use by people communicating with people. See and buy the Freedom line of Breaker antennas and accessories at your nearest electronic distributor. Look for the red, white and blue packaging.

WRITE FOR FREE CATALOG.

GEORGE WASHINGTON

West Coast Mirror Mount
 Dual Truck, RV Antennas
 Model 10-200

Weather resistant dual 57" stainless steel whip antennas with static arrestor tips. Secure horizontal or vertical mounting to West Coast side view truck type mirrors. Twin antennas co-phased for more directional power and easily adjustable for fine tuning. Hermetically sealed, white oversized ABS center load. Dual 18' low-loss coaxial phasing harnesses with solderless connectors and quick disconnect PL-259 plugs. Complete with corrosion resistant mounting hardware.

INDEPENDENCE

Gutter Mount Antenna
 Model 10-245

Low-profile 21" stainless steel whip antenna with static arrestor and flex-matic shock spring. Fits practically any vehicle rain gutter. No interference with door opening or passenger exit. Heavy-duty molded clamp bracket insulates and supports antenna. Center loaded ABS load coil for excellent transmission and reception. 14' coaxial cable with solderless connector and quick-disconnect PL-259 plug. Complete with corrosion resistant mounting hardware.

PAUL REVERE

Roof Mount Antenna
 Model 10-215

Special "power-plus" 42" base-loaded roof mount with long-life stainless steel whip, rugged stainless steel shock spring and high-quality 16-ft. shielded coax cable and solderless connections for fast "on-the-air" installation. Named after the famed communicator and hero of revolutionary era.

THE PATRIOT

Omni-directional
 ¼-Wave Base Antenna
 Model 11-101

High in quality, performance and efficiency, low in cost. Has three 108" quarter wave tubular aluminum radials plus a quarter-wave radiator (vertical element). Heavy-duty U-clamp fits mast up to 1½" diameter. Built-in lightning protector. SO-239 style connector mount. Mates with PL-259 plug. Shunt loaded coil. Heavy duty insulated molded clamp bracket. Easy to assemble and dis-assemble. Fixed construction.

THE MINUTEMAN

Trunk Mount Antenna Model 10-230


Sturdy, durable, no-hole required in trunk of vehicle. Super 44" stainless steel whip, base loaded low-profile antenna with stainless shock absorbing spring, chrome plated brass bell housing, 18-foot shielded coaxial cable and solderless connections.

"Just say it with Breaker!"



1101 Great Southwest Parkway
 Arlington, Texas 76011

CIRCLE NO. 53 ON FREE INFORMATION CARD

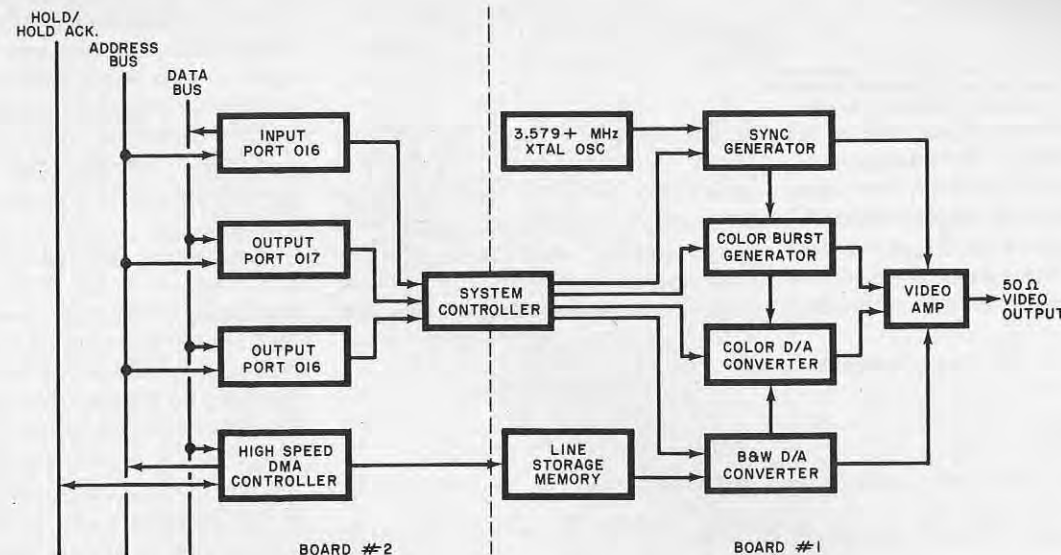

PARTS LIST

- | | | |
|---|---|---|
| C1 through C9, C18 through C25—0.1-μF disc ceramic capacitor | IC24—F3342DC 64 x 4 MOS shift register (Fairchild) | R8, R10—9100 ohms |
| C10, C11, C26, C27—47-μF, 20-volt tantalum capacitor | IC26—SN74151N 8-line to 1-line data selector | R9—18,000 ohms |
| C12—330-pF disc capacitor | IC34, IC46, IC54—SN74175N quadruple D-type edge-triggered flip-flop | R11—7500 ohms |
| C13—680-pF disc capacitor | IC36, IC53, IC55, IC61, IC63, IC64—SN7475N quadruple bistable latch | R12—15,000 ohms |
| C14, C15, C16—470-pF disc capacitor | IC38—SN7402N quadruple 2-input positive OR gate | R13—62,000 ohms |
| C17—9-35-pF variable capacitor | IC41—SN74LS10N triple 3-input positive NAND gate | R14—30,000 ohms |
| D1—1N914 silicon diode | IC44—SN74LS30N 8-input positive NAND gate | R15 through R20—13,000 ohms |
| D2—1N5242B, 12-volt zener diode | IC47—SN74LS08N quadruple 2-input positive AND gate | R21—820 ohms |
| IC1, IC37—LM340-5.0, 5-volt regulator | IC57—SN7495N 4-bit universal shift register | R22—1500 ohms |
| IC2, IC16, IC17, IC18—SN7410N triple 3-input positive NAND gate | IC58, IC59, IC65, IC72, IC73—SN74LS04N register | R23—330 ohms |
| IC3, IC10—SN7473N dual J-K master-slave flip-flop | IC60, IC62—SN7483N 4-bit binary full adder | R24—220 ohms |
| IC4, IC21, IC56—SN7432N quad 2-input OR gate | IC66, IC67, IC74—SN7405N hex inverter with open collector | R25—51 ohms |
| IC5, IC30—SN7430N 8-input positive NAND gate | IC68, IC69, IC70, IC71—SN74367 hex tri-state buffer | R26—100 ohms |
| IC6, IC23, IC42, IC43—SN7474N dual D-type edge-triggered flip-flop | Q1—2N3904 transistor | R27—22 ohms |
| IC7, IC19, IC35, IC40, IC48—SN7404N hex inverter | Q2, Q3—2N3906 transistor | R28—680 ohms |
| IC8, IC22, IC25, IC39, IC51—SN7408N quadruple 2-input positive AND gate | Following resistors are 5%, 1/4 watt: | R30, R31, R32—500-ohm trimmer potentiometers |
| IC9, IC14, IC15, IC28—SN7400N quadruple 2-input NAND gate | R1—150 ohms | XTAL—3.579545 MHz |
| IC11, IC12, IC31, IC32, IC49, IC50, IC52—SN7493N 4-bit binary counter | R2, R3—1000 ohms | Misc.—IC sockets (74), heat sinks (2), mounting hardware |
| IC13, IC27, IC33, IC45—SN74157N quadruple 2-input data selector | R4—470 ohms | Note: The following are available from Cromemco, 1 First St., Los Altos, CA 94022: complete set of parts less IC sockets at \$195; with IC sockets at \$215, assembled and tested Dazzler for \$350. California residents please include sales tax. Prices include postage for orders shipped within the U.S. Partial kits are not available. The schematic and foil patterns are available free of charge by sending a stamped (for 3 oz.) self-addressed 9" by 12" envelope to Cromemco, 1 First St., Los Altos, CA. 94022. |
| IC20, IC29—SN7420N dual 4-input positive NAND gate | R5, R6, R7, R29—1200 ohms | |

Fig. 1. Board 1 of the Dazzler contains an NTSC color TV signal generator with output through a 50-ohm line. Board 2 communicates with the computer and modulates the TV signal.

cost of a black-and-white terminal; and you do not need an RS-232 interface. The Dazzler can be built for less than \$200.

If you use your computer for business or accounting, the Dazzler can display multi-colored graphs of stored data. It can also be used to display a

picture produced by the Cyclops solid-state camera (POPULAR ELECTRONICS, February 1975). With the Cyclops picture either processed or unprocessed, the system can be used for security purposes, pattern recognition tests, and measurement and control of processes.

How It Works. A block diagram of the Dazzler is shown in Fig. 1. Most of the components on board #1 are used to generate a conventional NTSC (National Television Standards Committee) color video signal. The circuit is terminated in a 50-ohm, 1-volt output. This signal can be used to drive the

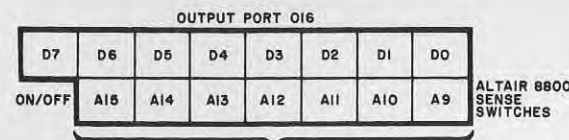


Fig. 2. Configuration of the data bits at output port 016.

video amplifier of a color set or to modulate a class-1 TV device connected to the set's antenna terminals (using a locally unoccupied channel).

The components on board #2 are used to communicate with the computer, with a high-speed DMA controller

as the basis. The controller issues a "hold" command when it is ready to access the computer memory. When the computer is ready, it issues a "hold acknowledge" command and the DMA begins operation.

Communication between the Daz-

Output Port 017

D7 - not used

D6 { 1 Resolution X4. Color and intensity set by D4 through D0.
0 Normal resolution (32 x 32 for 512 bytes, 64 x 64 for 2K bytes). Color and intensity set by 4-bit words in computer memory.

D5 { 1 Picture in 2K bytes of memory
0 Picture in 512 bytes of memory

D4 { 1 Color picture
0 Black-and-white picture

D3 { 1 High intensity color }
0 Low intensity color } Most significant bit of 4-bit B/W intensity

D2 { 1 Blue *
0 No blue

D1 { 1 Green *
0 No green

D0 { 1 Red
0 No red } Least significant bit

Fig. 3. The states of seven data bits at output port 017 determine resolution of TV picture and either chroma or monochrome parameters.

Memory Location	Memory Contents	Comments
000 000	076	Move immediate into
000 001	200	the accumulator.
000 002	323	Output to port
000 003	016	number 016.
000 004	333	Input
000 005	377	from sense switches.
000 006	323	Output to port
000 007	017	number 017.
000 010	303	Jump to
000 011	000	memory location 000
000 012	000	000.

Fig. 4. A test program to be used on the TV Dazzler.

zler and the host computer is through output ports 016 and 017 and input port 016. One bit of output port 016 is used to turn the Dazzler on and off, and the remaining seven bits are used to set the starting address of the picture in the computer memory. The organization of output port 016 is shown in Fig. 2.

Output port 017, whose organization is shown in Fig. 3, is used to set the format of the TV picture. Note that bit D7 is not used. Bit D6 is used to set normal resolution (32 x 32 for 512 bytes or 64 x 64 for 2K bytes) or 4X resolution (64 x 64 for 512 bytes or 128 x 128 for 2K bytes). Bit D5 sets the amount of computer memory, starting at the location given to output port 016, allocated to the picture. When 512 bytes are selected, the computer memory must have an access time of at least one microsecond. When 2K bytes are used, the memory must have an access time of at least 500 nanoseconds.

Bit D4 is used to select either a black-and-white or color display. In the 4X resolution mode (D6 at a 1), bits D3 to D0 are used to set the color of the display when in the color mode or the intensity when D4 is in the black-and-white mode. Bits D3 to D0 are not used in the normal resolution mode.

Only two bits of input port 016 are used. When bit D7 is a 1 (high), it indicates that the Dazzler is enabled (bit D7 of output port 016 actually performs the enabling), while bit D6 goes low to indicate an end of frame. This latter bit is useful when changing frames in rapid succession.

To generate a TV picture with the Dazzler, the information that the Dazzler reads from the computer memory must be properly formatted. In the 4X resolution (output port 017, bit D6 high), each point on the TV screen is controlled by just one bit in the computer memory. This bit turns its corresponding point in the picture on or off. The color or intensity of that frame of the picture is set by bits D3 through D0 of the control word at output port 017. To get full color in the 4X mode, multiple frames of different colors must be interleaved.

In the normal resolution mode (output port 017, bit D6 low), the color and intensity of each point on the screen is controlled by a four-bit "nybble" in the computer memory. Two points of the picture are thus encoded in each byte of the computer memory. For this reason, a 64 x 64 picture requires 2K of

POPULAR ELECTRONICS

THE GAME OF LIFE

One of the most fascinating uses of the Dazzler is in playing what is known as "The Game of Life." (See *Scientific American*, October 1970, p 120; February 1971, p 112; April 1971, p 116.) The game is started by entering the program shown below. (A paper tape of the program is available for \$15 from Cromemco, 1 First St., Los Altos, CA 94022.) Then a colony of cells is entered to appear on the TV screen on a 64 x 64 grid.


Each cell in the colony has eight possible neighbors, as shown at right. The evolution of the colony proceeds according to a fixed set of rules invented by John Conway at the University of Cambridge. Every cell with two or three neighbors will survive to the next generation. Every cell with four or more neighbors dies from over-population. Every cell with one neighbor or no neighbors dies from isolation. Every cell with exactly three neighbors is a birth cell—a new cell is born here in the subsequent generation.

In the Dazzler version of The Game of Life, blue represents life; birth generates a green cell; and death is shown in red. There are many surprises to be found in the game. Some colonies survive and prosper; others reach a stable state—neither grow-

ing nor lessening. Other colonies fade from existence. Some colonies, known as "gliders" sail across the screen and can be devoured by other colonies in the process.

The full-color illustrations on the first page of this article are actual photos of a TV screen several generations into a Life program.

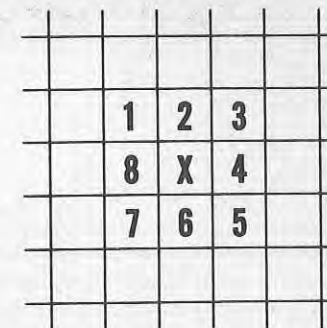The initial colony of cells is drawn on the TV screen using ASCII keyboard inputs as controls. Control A deposits a cell of life on the screen. Controls N, O, P, and H step the cursor up, down, right, and left, respectively. Once the initial colony is complete, Control D is initiated to start the game.



Each cell has 8 possible neighbors.

Program for Game of Life is below.

DAZZLE-LIFE PROGRAM (LOADS BEGINNING 000 000, RUNS FROM 000 000)

OCTAL LISTING (000 000 = 061, 000 001 = 000, 000 002 = 010 ETC.)

memory storage. The lowest order (D0) bit determines if the display is red, D1 is green, D2 is blue, and D3 determines either a high- or low-intensity color. In black and white, these four bits are used to determine one of 16 shades of gray.

Construction. The Dazzler consists of two adjoining pc boards that plug directly into the Altair-8800 bus connectors. The video output is taken from a pad on board #1. The schematics, etching and drilling guide and component placement diagram for the boards are too large for reproduction here. They can be obtained FREE by sending a stamped, self-addressed 9" by 12" envelope to Cromemco, 1 First St., Los Altos, CA 94022. (These items are also included with each kit as mentioned in the Parts List.)

In assembling the pc boards, note that all components are mounted on one side of the board, with all soldering on the opposite side. The sides to be soldered are those on which the foil marking can be properly read. Plated-through holes assure contact on the component side. If desired, sockets can be used for mounting the IC's. When soldering, use a low-wattage iron and fine solder. Inspect your work

CALCULATE YOURSELF A NICE SAVINGS ON POPULAR ELECTRONICS
33% OFF NEWSSTAND PRICE

SAVE \$3⁰¹ with this introductory offer for new subscribers.

Sound like a good deal? It is! You pay only \$5.99 for a year's subscription, instead of the regular yearly price of \$6.98! Punch that up on a calculator and you'll see that's a savings of 33% off annual newsstand price of \$9.00.

So why wait? Plug in to a great deal today. Get 12 issues (1 year) of Popular Electronics for just \$5.99. Or save even more: get 2 years (24 issues) for only \$11.98. Simply fill out, detach and mail the certificate at right. Prompt Delivery—your first issue will be shipped 30-60 days from receipt of your order.



FOR NEW SUBSCRIBERS

GOOD FOR \$3.01 OFF

Popular Electronics

P.O. Box 2774, Boulder, Colo. 80302

- Send me a full year—12 issues—of Popular Electronics for just \$5.99—33% off annual newsstand price of \$9.00.
 I want to save even more. Send me two years—24 issues—for just \$11.98.

CHECK ONE: Please bill me. Payment enclosed (please mail this form in an envelope).

MR./MRS./MS. _____ (please print) 4S07

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Additional postage per year: add \$1.00 for Canada; \$2.00 for all countries outside the U.S.

FOR NEW SUBSCRIBERS ONLY

12 MONTHS FOR \$5.99

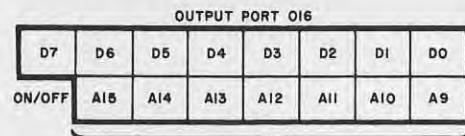


Fig. 2. Configuration of the data bits at output port 016.

STARTING ADDRESS OF PICTURE IN MEMORY
video amplifier of a color set or to modulate a class-1 TV device connected to the set's antenna terminals (using a locally unoccupied channel).

The components on board #2 are used to communicate with the computer, with a high-speed DMA controller

as the basis. The controller issues a "hold" command when it is ready to access the computer memory. When the computer is ready, it issues a "hold acknowledge" command and the DMA begins operation.

Communication between the Daz-

Output Port 017

D7 - not used

D6 { 1 Resolution X4. Color and intensity set by D4 through D0.
0 Normal resolution (32 x 32 for 512 bytes, 64 x 64 for 2K bytes). Color and intensity set by 4-bit words in computer memory.

D5 { 1 Picture in 2K bytes of memory
0 Picture in 512 bytes of memory

D4 { 1 Color picture
0 Black-and-white picture

D3 { 1 High intensity color } ----- Most significant bit of
0 Low intensity color } 4-bit B/W intensity

zler and the host computer is through output ports 016 and 017 and input port 016. One bit of output port 016 is used to turn the Dazzler on and off, and the remaining seven bits are used to set the starting address of the picture in the computer memory. The organization of output port 016 is shown in Fig. 2.

Output port 017, whose organization is shown in Fig. 3, is used to set the format of the TV picture. Note that bit D7 is not used. Bit D6 is used to set normal resolution (32 x 32 for 512 bytes or 64 x 64 for 2K bytes) or 4X resolution (64 x 64 for 512 bytes or 128 x 128 for 2K bytes). Bit D5 sets the amount of computer memory, starting at the location given to output port 016, allocated to the picture. When 512 bytes are selected, the computer memory must have an access time of at least one microsecond. When 2K bytes are used, the memory must have an access time of at least 500 nanoseconds.

Bit D4 is used to select either a black-and-white or color display. In the 4X resolution mode (D6 at a 1), bits D3 to D0 are used to set the color of the display when in the color mode or the intensity when D4 is in the black-and-white mode. Bits D3 to D0 are not

THE GAME OF LIFE

One of the most fascinating uses of the Dazzler is in playing what is known as "The Game of Life." (See *Scientific American*, October 1970, p 120; February 1971, p 112; April 1971, p 116.) The game is started by entering the program shown below. (A paper tape of the program is available for \$15 from Cromemco, 1 First St., Los Altos, CA 94022.) Then a colony of cells is entered to appear on the TV screen on a 64 x 64 grid.


Each cell in the colony has eight possible neighbors, as shown at right. The evolution of the colony proceeds according to a fixed set of rules invented by John Conway at the University of Cambridge. Every cell with two or three neighbors will survive to the next generation. Every cell with four or more neighbors dies from over-population. Every cell with one neighbor or no neighbors dies from isolation. Every cell with exactly three neighbors is a birth cell—a new cell is born here in the subsequent generation.

In the Dazzler version of The Game of Life, blue represents life; birth generates a green cell; and death is shown in red. There are many surprises to be found in the game. Some colonies survive and prosper; others reach a stable state—neither grow-

ing nor lessening. Other colonies fade from existence. Some colonies, known as "gliders" sail across the screen and can be devoured by other colonies in the process.

The full-color illustrations on the first page of this article are actual photos of a TV screen several generations into a Life program.

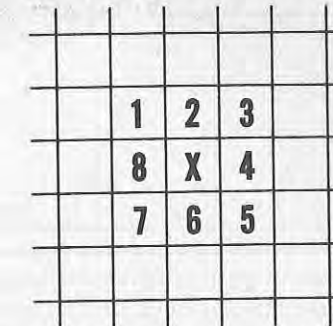The initial colony of cells is drawn on the TV screen using ASCII keyboard inputs as controls. Control A deposits a cell of life on the screen. Controls N, O, P, and H step the cursor up, down, right, and left, respectively. Once the initial colony is complete, Control D is initiated to start the game.



Each cell has 8 possible neighbors.

Program for Game of Life is below.

DAZZLE-LIFE PR0GRAM (LOADS BEGINNING 000 000, RUNS FROM 000 000)

OCTAL LISTING (000 000 = 061, 000 001 = 000, 000 002 = 010 ETC.)

```

061 000 010 315 265 001 315 335 001 315 175 000 315 142 000 315
222 000 315 142 000 333 377 027 332 125 000 027 332 106 000 303
111 000 311 002 002 002 002 002 002 002 002 002 002 002 002
002 002 002 002 002 002 002 002 002 002 002 002 311 001 000 000
315 324 000 076 100 014 271 302 200 000 016 000 004 270 302 200
000 311 001 000 000 315 064 001 376 011 302 245 000 076 000 315
105 001 303 257 000 376 012 302 257 000 076 004 315 105 001 076
100 014 271 302 225 000 016 000 004 270 302 225 000 311 041 000
010 021 000 370 006 000 076 000 272 302 316 000 273 310 160 023
043 303 310 000 305 076 000 271 302 354 000 015 315 034 001 062
164 002 301 305 315 034 001 062 165 002 301 305 014 315 034 001
041 165 002 106 167 200 053 116 160 201 127 301 310 325 315 064
001 321 376 000 312 023 001 172 376 003 310 376 004 310 076 011
303 105 001 172 376 003 300 076 012 303 105 001 005 303 176 002
004 315 052 001 004 315 052 001 172 311 325 315 064 001 321 376
000 303 206 002 315 141 001 176 332 076 001 346 017 311 346 360
007 007 007 007 311 346 017 365 315 141 001 321 332 125 001 176
346 360 202 167 311 172 007 007 007 007 127 176 346 017 202 167
311 041 000 010 170 346 040 312 156 001 021 000 002 031 171 346
040 312 170 001 021 000 004 031 171 346 037 007 007 007 027 137
076 000 027 127 031 170 037 365 346 017 137 026 000 031 361 311
333 000 346 040 300 014 302 220 001 004 302 220 001 311 333 000
346 002 312 236 001 170 323 001 311 106 076 000 270 310 315 236
001 043 303 251 001 315 276 000 076 204 323 016 076 260 323 017
041 163 002 315 251 001 315 220 001 312 306 001 333 001 107 315
236 001 346 177 376 131 310 043 163 002 303 236 001 043 163 002
315 236 001 303 214 002 315 102 002 303 166 002 127 227 276 312
346 001 172 276 312 375 001 043 043 043 303 355 001 043 136 043
126 353 315 010 002 303 346 001 351 001 062 002 071 002 004
050 002 010 100 002 011 067 002 017 060 002 013 052 002 015 056
002 016 076 002 000 000 000 000 301 311 021 000 000 311 006 000
014 311 076 017 315 105 001 004 311 076 000 303 064 002 015 311
005 311 315 064 001 365 305 076 014 315 105 001 021 370 370 315
220 001 302 157 002 301 305 076 000 315 105 001 021 370 370 315
220 001 301 312 106 002 361 315 105 001 333 001 323 001 311 301
303 146 002 000 000 000 041 011 002 346 177 303 354 001 026 000
315 052 001 303 040 001 310 376 012 310 024 311 315 276 000 021
000 000 303 346 001 000 000 000 000 000 000 000 000 000 000

```

FEBRUARY 1976

memory storage. The lowest order (D0) bit determines if the display is red, D1 is green, D2 is blue, and D3 determines either a high- or low-intensity color. In black and white, these four bits are used to determine one of 16 shades of gray.

Construction. The Dazzler consists of two adjoining pc boards that plug directly into the Altair-8800 bus connectors. The video output is taken from a pad on board #1. The schematics, etching and drilling guide and component placement diagram for the boards are too large for reproduction here. They can be obtained FREE by sending a stamped, self-addressed 9" by 12" envelope to Cromemco, 1 First St., Los Altos, CA 94022. (These items are also included with each kit as mentioned in the Parts List.)

In assembling the pc boards, note that all components are mounted on one side of the board, with all soldering on the opposite side. The sides to be soldered are those on which the foil marking can be properly read. Plated-through holes assure contact on the component side. If desired, sockets can be used for mounting the IC's. When soldering, use a low-wattage iron and fine solder. Inspect your work to make sure you have no solder bridges.

Because portions of the Dazzler operate at very high frequencies, it is important that all components be mounted close to the pc board. Be sure to use components that meet the required specifications—some untested IC's may not have the required switching speeds.

There are 36 IC's on board 1, plus the color crystal oscillator, and associated passive components. A heat sink is used for IC1, the 5-volt regulator on board #1. When mounting the color-burst crystal, use a small length of wire soldered from the metal case of the crystal to the ground foil immediately above the case. This reduces noise pickup.

One of the center dual in-line positions in the bottom row of board #1 is used for board-to-board interconnections rather than an IC.

There are 37 IC's on board #2. One dual in-line position is left open for interconnections. To connect the two boards, use sixteen 8" lengths of insulated wire (or a 16-conductor flat cable).

The two boards are attached using 5/8" spacers at each corner hole, with



Check out this savings on Popular Electronics

33% OFF

the newsstand price

Tally up a nice savings! Get a full year of Popular Electronics for just \$5.99. A full year of our test reports on new equipment. Tips on building your own equipment. Plus special stereo, hobby, solid-state and CB features to boot!

So go ahead! Get a full year (12 issues) of Popular Electronics for just \$5.99. Or get two years (24 issues) for only \$11.98—and save even more. Just complete, detach and mail the postpaid reply card at left.

FIRST CLASS
Permit No. 906
Boulder, Colo.

BUSINESS REPLY MAIL

No Postage Stamp Necessary If Mailed In The United States

POSTAGE WILL BE PAID BY

Popular Electronics

P.O. Box 2774
Boulder, Colorado 80302

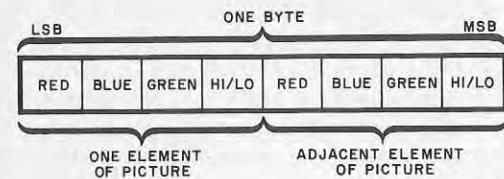


Fig. 5. In low-resolution mode, four bits of computer memory are used for each picture element.

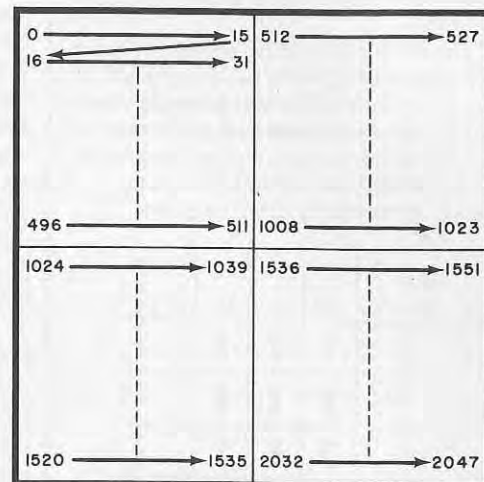


Fig. 6. Memory map of the Dazzler picture. Only first quadrant is displayed in the 512-byte display. All four are displayed in 2K-byte picture.

the component side of one facing the soldered side of the other. The two are separated by exactly the same distance as two adjacent connectors on the Altair bus.

Check-Out. Check for solder bridges and proper component orientation. Facing the component side of a board, pin 1 of each IC should be at the lower left. Check the interconnections between the boards.

Turn off the power to the Altair and then insert the Dazzler into adjacent sockets on the bus line. Using a length of coaxial cable, connect the Dazzler video output (ground the coax braid to

the adjacent ground foil) to the video input and signal ground of your color TV receiver. The connection can usually be made at the input to the video amplifier, with a switch to select the normal input or the Dazzler input.

Tune-Up. The Dazzler is activated and deactivated by software control. The simple program shown in Fig. 4 will turn the Dazzler on and display a picture that is stored starting at location zero in memory (D0 through D6 of output port 016 at zero). This short program also allows sense switch control of the word sent to output port 017. The sense switches are labelled

A8 through A15 on the front panel of the Altair.

Load from the program in Fig. 4 into the Altair from the front panel, examine zero and run the program beginning at location zero in memory. (Be sure all sense switches are down.)

With the color TV set operating and the Altair "running", raise sense switch A12 and note that a colorful quilt-like pattern appears on the screen. Potentiometer R30 (bias) on board 1 of the Dazzler acts as a horizontal hold control and should be adjusted to obtain a stable picture.

Raise sense switches A10 and A11, and adjust capacitor C17 on board #1 for the most saturated blue on the screen. Now put A10 down, raise A9, and adjust R32 for the most saturated green color. Finally, set A9 down, raise A8, and adjust R32 for the most saturated red color.

Dazzler Software. When writing programs for the Dazzler, it is important to remember that the TV picture is stored as a specially coded sequence in the computer memory. The Dazzler simply interprets this code to form the TV image.


Two different codes are used depending on whether the Dazzler is in the low-resolution or high-resolution mode. This is determined by the control word at output port 017. In the low-resolution mode, four bits of computer memory are used to code each element of the picture (Fig. 5). Either a 32 x 32 or 64 x 64 element picture can be displayed. The latter is organized as quadrants within the computer memory as shown in Fig. 6.

In the high-resolution mode, each bit of memory is used either to turn on



Fig. 7. In high-resolution mode, each memory byte is used to represent 8 picture elements.

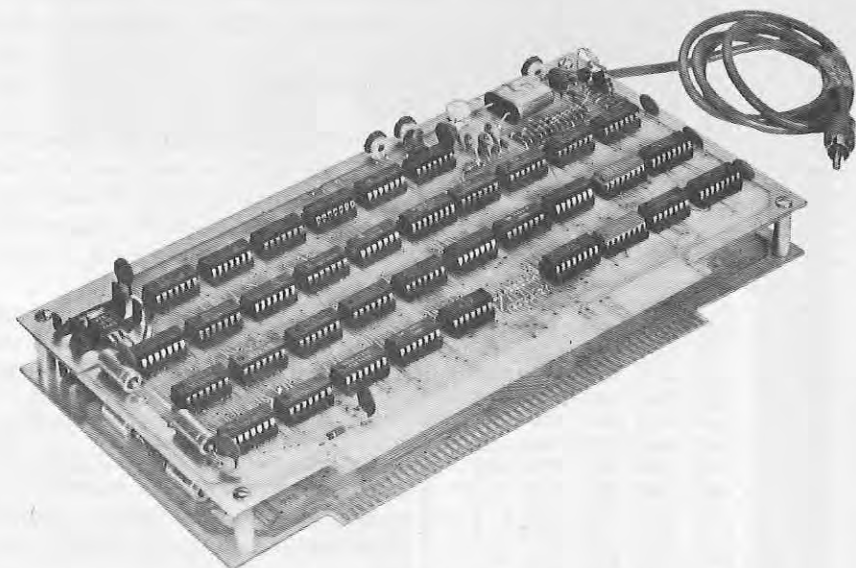(bit=1) or off (bit=0) a single memory element. The control word output to port 017 is used to set the picture color. Figure 7 shows how one byte of memory is divided up to control eight elements of the picture. In this mode, either a 64 x 64 element picture using 512 bytes or a 128 x 128 element picture using 2K bytes can be displayed on the screen. ♦




The Dazzler fits in two slots on the Altair bus. Output is video and can be fed to amplifier of TV set or an FCC-approved class-1 r-f device.


THE NEW 1976 COLOR TV RECEIVERS

Serviceability and automatic color controls are emphasized in most lines.

BY ART MARGOLIS

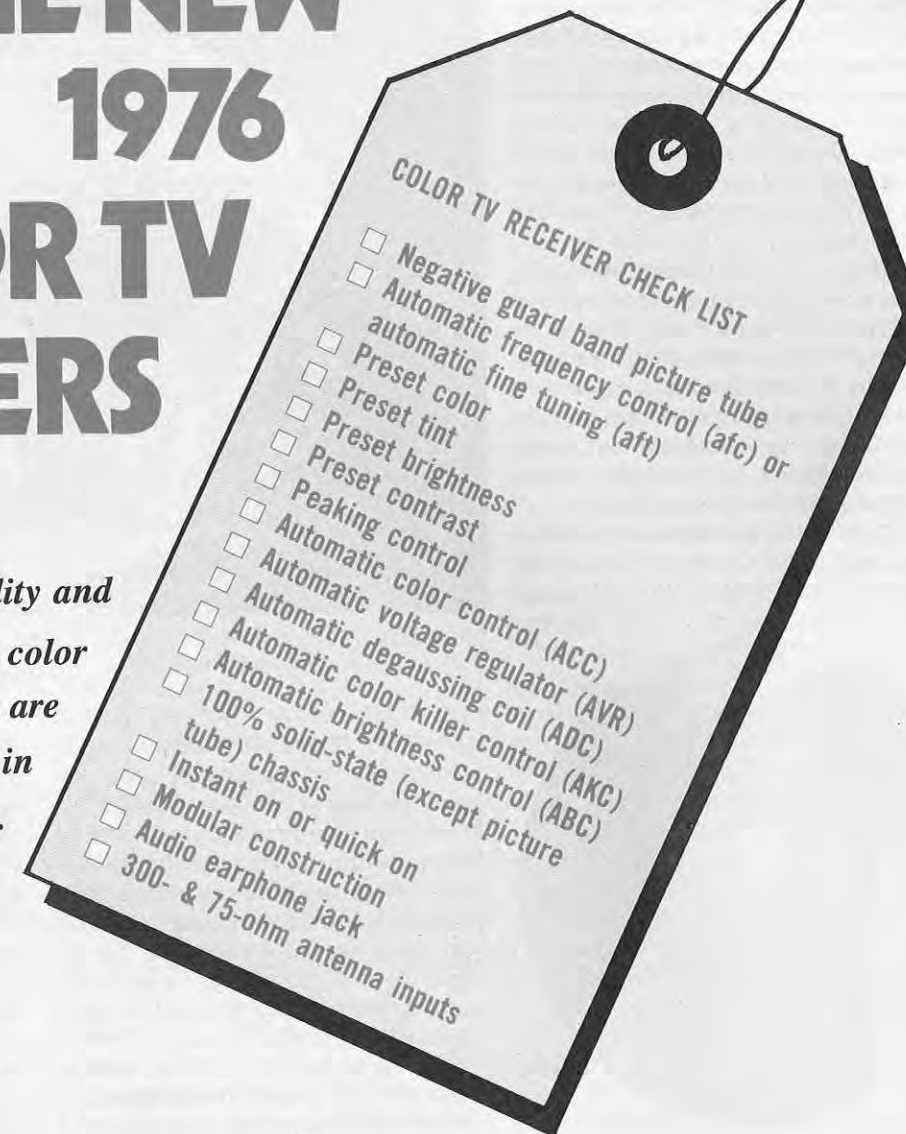

- COLOR TV RECEIVER CHECK LIST**
- Negative guard band picture tube
 - Automatic frequency control (afc) or automatic fine tuning (aft)
 - Preset color
 - Preset tint
 - Preset brightness
 - Preset contrast
 - Peaking control
 - Automatic color control (ACC)
 - Automatic voltage regulator (AVR)
 - Automatic degaussing coil (ADC)
 - Automatic color killer control (AKC)
 - 100% solid-state (except picture tube) chassis
 - Instant on or quick on
 - Modular construction
 - Audio earphone jack
 - 300- & 75-ohm antenna inputs

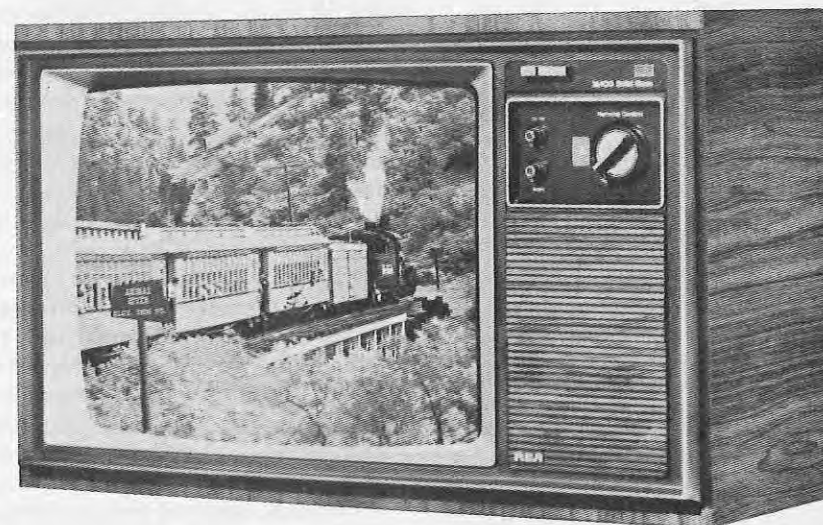

The RCA line of XL-100 receivers features ColorTrak, a remote Control Center which operates all primary controls.

In the 30 years since television first became a serious entertainment medium, TV receiver design has come full circle. Some TV receivers started out in modular form and now most of them have come back to this practical method of assembly, prompted mainly by a need for simple, efficient servicing. High on the list of desirable features for modern TV receivers are modular circuit assemblies, featuring, in many cases, active components that plug in and out for easy replacement.

Just as the auto industry has become accustomed to introducing new model cars each year, TV receiver manufacturers think in the same terms. Each year sees new features incorporated into existing models and completely new models coming on the market. An example of the former is